

SHRI S.H.KELKAR COLLEGE OF ARTS, COMMERCE & SCIENCE, DEVGAD
FIRST TERM END EXAMINATION
USPH302



MAX.MARKS:75

DURATION: 2 HOURS

- N.B (i) All questions are compulsory.
(ii) Figures to the right indicate full marks.
(iii) Use of non-programmable calculator is allowed.

Q 1.A) Attempt any One.

08

1. What are the methods of transistor biasing? Explain base resistor bias.
2. What are the types of feedback of amplifiers? And give general theory of feedback.

B) Attempt any One.

08

1. Explain the stabilisation and its need for the transistor.
2. Explain the following terms in relation to amplifiers
i) input resistance ii) output resistance

C) Attempt any One.

04

1. In collector feedback biased silicon transistor circuit. $R_c=1K$, $R_b=120K$ and $\beta=100$. Determine the operating point if $V_{CC}=+12V$
2. It is desired to set the operating point at $4V$, 1.2 mA by biasing silicon transistor with collector feedback resistor R_B . If $\beta=120$, find the value of R_B .

Q. 2. A) Attempt any One.

08

1. Explain phase shift oscillator
2. By means of a neat circuit diagram explain the working of Op-amp as Integrator. Derive the necessary relation

B) Attempt any One.

08

1. Write a note on requirements of sustained oscillators.
2. Explain non-inverting amplifier.

C) Attempt any One.

04

1. A colpitt's oscillator is designed by using the following passive component, $C_1=0.02\text{ }\mu\text{F}$, $C_2=0.002\text{ }\mu\text{F}$ and $L=10\text{ }\mu\text{H}$. calculate oscillating frequency.
2. In a typical circuit of Wien bridge oscillator, what should be the value of R when the frequency of 1 KHz is required with $C=0.1\text{ }\mu\text{F}$? If R_3 is 1.5 K , what must be the value of R_4 ?

Q.3 A) Attempt any One.

08

1. State the difference between latch and flipflop
2. Explain the types of registers in brief.

B) Attempt any One.

08

1. With circuit diagram explain edge triggered JK flipflop
2. Explain the types of the counters.



C) Attempt any One.

1. Explain parallel in parallel out (PIPO) shift register.
2. Explain clocked pulses in flipflop.

(04

Q.4. Attempt any **Three**

15

1. Write a note on conditions of faithful amplification.
2. Determine the open circuit voltage of the source, v_s to provide an amplifier input voltage v_i of 0.25 volt when the internal resistance of the source is 50ohms.
3. Determine the maximum frequency that may be used for an opamp with slew rate 0.5 V/ μ s. the circuit has $R_f=240\text{Kohm}$, $R_i= 10\text{Kohm}$ and input voltage $v_i=0.02\text{V}$ having angular frequency $\omega=300\times 10^3$ rad/s.
4. What are the effects of positive feedback in oscillators?
5. Write a note on flipflop.
6. Explain parallel in serial out shift register. (PISO)